

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Supplementary Summer Examination – 2023

Course: B. Tech. Branch : Electrical Engineering Semester : VII

Subject Code & Name: Electrical Drives (BTEEC703)

Max Marks: 60

Date:18/07/2023

Duration: 3 Hr.

Instructions to the Students:

1. *All the questions are compulsory.*
2. *The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.*
3. *Use of non-programmable scientific calculators is allowed.*
4. *Assume suitable data wherever necessary and mention it clearly.*

(Level/CO) Mark

Q. 1 Solve Any Two of the following.

12

- | | | |
|---|---------------|----------|
| A) What are the different types of torque that involved in drive system? | Understanding | 6 |
| B) Explain four quadrant operation of motor drive system with hoist load. | Understanding | 6 |
| C) What are the modes of operation in electric drive system? | Applying | 6 |

Q.2 Solve Any Two of the following.

12

- | | | |
|---|---------------|----------|
| A) Explain the operation of closed loop speed control with inner current control loop and What are the methods used in current sensing. | Understanding | 6 |
| B) Explain a phase locked loop speed control schemes? Where do you use it? | Applying | 6 |
| C) Write a brief note on classes of duty for on electric motor in on electric drive | Understanding | 6 |

Q. 3 Solve Any Two of the following.

12

- | | | |
|---|---------------|----------|
| A) Explain any two methods of braking of DC Shunt Motors with neat diagrams. | Understanding | 6 |
| B) Explain with neat sketches about the DC Shunt Motor speed control by using single phase fully controlled bridge converter. | Applying | 6 |

- C) A single phase bridge converter fed from a 250 V, 50 Hz supply is used to control the speed of a separately excited dc motor having an armature resistance of 1.5Ω and inductance 30 mH. The back emf at one speed of operation is 100 V and the converter control angle is 30° . Determine the average and rms values of the armature current, the power input to the motor and power factor of operation **6**

Q.4 Solve Any Two of the following. **12**

- A) Explain with neat diagram voltage source inverter fed Induction motor drive Understanding **6**
- B) A slip ring induction motor incorporating slip energy recovery scheme for speed control drives a fan load having a characteristic of $T_L = KN^2$. The motor is rated at 440 V, 50 Hz, 100 kW. The speed is to be controlled from a rated value of 1420 to 750 rpm. The equivalent circuit parameters are $r_1 = 0.052 \text{ ohm}$, $r_2 = 0.06 \text{ ohm}$, $X_m = 10 \text{ ohm}$, $x_1 + x'_2 = 0.29 \text{ ohm}$, $\frac{T_P}{T_S} = 1.2$ Determine the firing angle range. Applying **6**
- C) Explain in brief drives required for various stages in textile mills **6**

Q.5 Solve Any Two of the following. **12**

- A) Explain in detail drives for cement mills application. Understanding **6**
- B) Draw the block diagram of variable frequency control of multiple synchronous motor drive and explain in brief. Understanding **6**
- C) Describe the static Kramer drive for speed control of 3-phase Slip ring IM. Draw and explain the speed torque characteristics of static Kramer drive? Understanding **6**

*** End ***