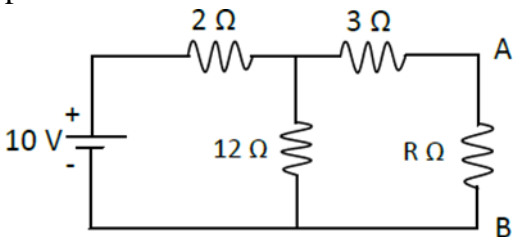
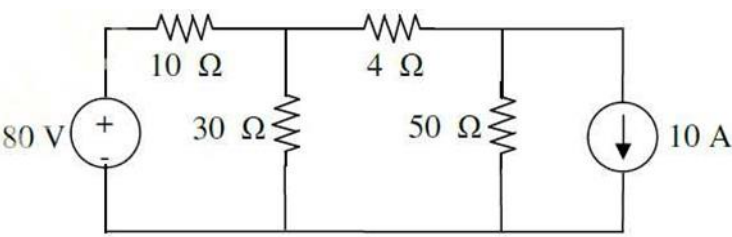
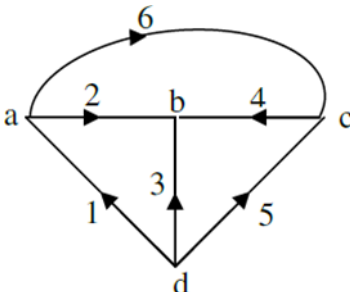
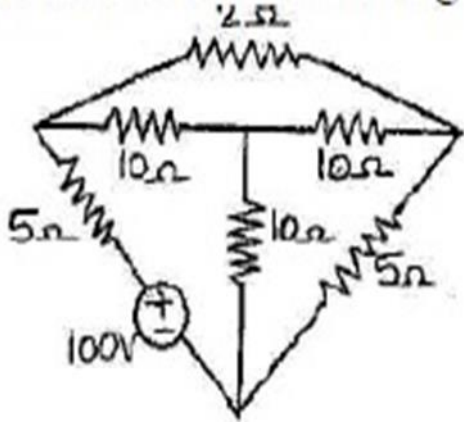
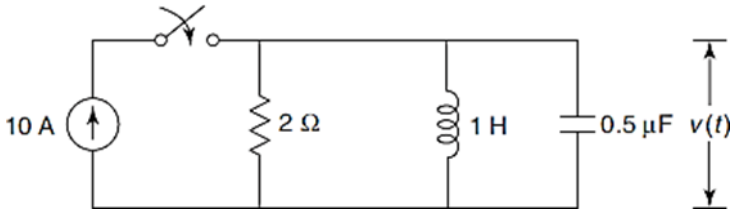
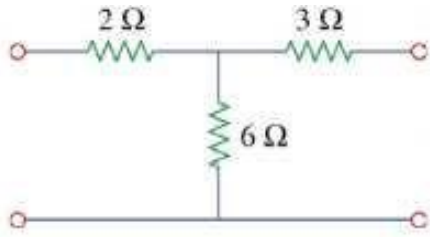
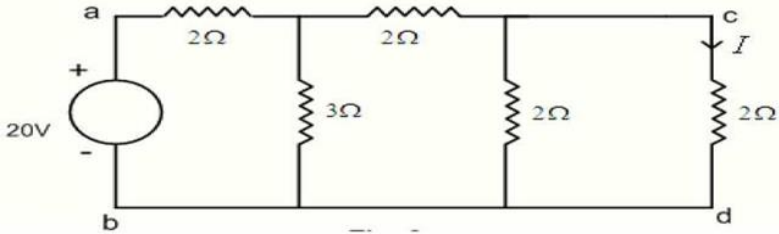
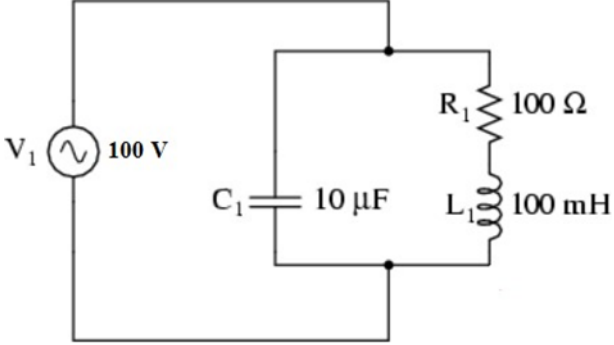


<b>DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE</b> <b>Supplementary Examination – Summer 2022</b> <b>Course: B. Tech.                      Branch :Electrical Engineering                      Semester :III</b> <b>Subject Code &amp; Name: Network Analysis and Synthesis (BTEEC302)</b> <b>Max Marks: 60                              Date:                              Duration: 3 Hr.</b>			
<b>Instructions to the Students:</b> 1. All the questions are compulsory. 2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in ( ) in front of the question. 3. Use of non-programmable scientific calculators is allowed. 4. Assume suitable data wherever necessary and mention it clearly.			
		(Level/CO)	Marks
<b>Q. 1</b>	<b>Solve Any Two of the following. (This is just a sample instruction)</b>		
<b>A)</b>	Find the maximum power delivered to the load by using maximum power transfer theorem for the following circuit. 	(CO2)	6
<b>B)</b>	Verify Superposition theorem for 4Ω resistor for the following circuit. 	(CO2)	6
<b>C)</b>	Explain the following terms: i) Independent and Dependent sources ii) Lumped and Distributed Systems	(CO1)	6
<b>Q.2</b>	<b>Solve Any Two of the following. (This is just a sample instruction)</b>		
<b>A)</b>	Explain Dot convention with suitable example	(CO2)	6
<b>B)</b>	For the graph shown below find incidence and cut set matrices 	(CO2)	6
<b>C)</b>	Explain the concept of Super-mesh and Super-node with one suitable example for each.	(CO2)	6

<b>Q. 3</b>	<b>Solve Any Two of the following.</b> <i>(This is just a sample instruction)</i>		
A)	Explain the complete response of source free series RLC Circuits	(CO4)	6
B)	Draw the dual network of given network. 	(CO2)	6
C)	For the network shown in Fig., the switch is closed at $t = 0$ , determine $v$ , $dv/dt$ , and $d^2v/d^2t$ at $t = 0+$ . 	(CO2)	6
<b>Q.4</b>	<b>Solve Any Two of the following.</b> <i>(This is just a sample instruction)</i>		
A)	Find the ABCD parameters for the following circuit. 	(CO2)	6
B)	What is a filter? Explain about various types of filters.		6
C)	A series RLC circuit with $R = 2$ ohm, $L = 1$ H and $C = 0.5$ Farad with the applied voltage $V(t) = \sin t$ . Find $i(t)$ if the switch is closed at $t = 0$ . Use Laplace transform method.	(CO2, CO3)	6
<b>Q. 5</b>	<b>Solve Any Two of the following.</b> <i>(This is just a sample instruction)</i>		
A)	Verify the reciprocity theorem for the network shown in fig	(CO2)	6

			
B)	<p>Write the property of laplace transform  1) Unit impulse 2) Unit step and 3) Unit ramp function</p>	(CO3)	6
C)	<p>In a parallel Resonant circuit shown in figure find  1) The Resonant frequency 2) Bandwidth 3) Q-factor</p> 	(CO4)	6
*** End ***			

The grid and the borders of the table will be hidden before final printing.