

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE			
Supplementary Examination – Summer 2022			
Course: B. Tech.	Branch : EE	Semester :6	
Subject Code & Name: BTEEC603 & Power Electronics			
Max Marks: 60	Date:	Duration: 3 Hr.	
Instructions to the Students:			
<ol style="list-style-type: none"> 1. All the questions are compulsory. 2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question. 3. Use of non-programmable scientific calculators is allowed. 4. Assume suitable data wherever necessary and mention it clearly. 			
		(Level/CO)	Marks
Q. 1	Solve Any Two of the following.		
A)	Define (i) Latching Current (ii) Holding current (iii) Forward Break Over voltage		6
B)	With the help of neat waveforms explain V-I characteristics of MOSFET		6
C)	Discuss different triggering methods of SCR		6
Q.2	Solve Any Two of the following.		
A)	With the help of neat circuit diagram & waveforms explain operation single phase half wave controlled rectifier with R Load		6
B)	Explain difference between Semi converter & Full converter		6
C)	List out the advantages of Freewheeling diode		6
Q. 3	Solve Any One of the following.		
A)	Draw a neat circuit diagram of three phase bridge Inverter and with the help of neat waveforms explain 180 degree mode of operation		12
B)	Draw a neat circuit diagram and explain operation of Buck regulator & also derive its output voltage equation		12
Q.4	Solve Any Two of the following.		
A)	What is step down chopper? Derive its output voltage equation & prove it.		6
B)	Discuss different control strategies used in choppers		6
C)	List out advantages & applications of chopper		6
Q. 5	Solve Any One of the following.		

A)	Draw a neat circuit diagram of single phase Stepdown Cycloconverter & with neat waveforms explain its operation		12
B)	Write a note on single phase dual converter		12
	*** End ***		

The grid and the borders of the table will be hidden before final printing.